




**UNIVERSIDAD
DE BURGOS**

Lesson 2: Logic families

José M. Cámara and Miguel Cantera


(checam@ubu.es and macantera@ubu.es)

V 1.2

 

Integration Scale

- According to the number of transistors (or logic gates) integrated into an integrated circuit, devices are classified into the following categories:
 - SSI (small-scale integration): 3 – 30
 - MSI (medium-scale integration): 30 – 300
 - LSI (large-scale integration): 300 – 3,000
 - VLSI (very large-scale integration) > 3,000
 - ULSI (ultra large-scale integration) > 1,000,000
- Lithographic resolution (minimum feature size) has improved in parallel:
 - Submicron technology: $L_{\min} \geq 0,35\mu\text{m}$
 - Deep-submicron technology: $0,1\mu\text{m} \leq L_{\min} \leq 0,35\mu\text{m}$
 - Ultra-deep-submicron technology: $L_{\min} \leq 0,1\mu\text{m}$

 

Key Parameters

- Supply Voltage.
- Logic Levels.
- Noise Margin.
- Current Ratings.
- Propagation Delay.
- Fan-Out.
- Power Dissipation.
- Speed–Power Product.

Supply Voltage

The supply voltage range that guarantees proper device operation.

Symbol	Parameter	Series	Min	Typ	Max	Unit
V_{CC}	Supply Voltage	54 74	4.5 4.75	5.0 5.0	5.5 5.25	V


If $V_{CC} < \text{Min.}$, the device may not operate as specified.

If $V_{CC} > \text{Max.}$ the device may be permanently damaged.

If $\text{Min.} < V_{CC} < \text{Max.}$, the manufacturer guarantees proper operation.

Logic Levels

 Logic levels define the voltage ranges corresponding to logic '0' and logic '1'. Rather than fixed values, these levels are specified as voltage ranges. They depend on the supply voltage, particularly in **CMOS** logic families, which support a wide operating voltage range.



V_{iH} : Minimum input voltage recognized as a logic HIGH.
 V_{iL} : Maximum input voltage recognized as a logic LOW.

V_{oH} : Minimum output voltage for a logic HIGH.

V_{oL} : Maximum output voltage for a logic LOW.

Symbol	Parameter	Limits			Unit
		Min	Typ	Max	
V_{iH}	Input High Voltage	2.0			V
V_{iL}	Input Low Voltage			0.8	V
V_{oH}	Output High Voltage	2.7	3.5		V
V_{oL}	Output Low Voltage		0,25	0.4	V

When two devices operate with different logic voltage levels, their inputs and outputs may be incompatible. This may result in improper operation (if the input threshold is not reached) or even damage the device (if the maximum allowable voltage is exceeded).

A common example is connecting a sensor to a microcontroller or microprocessor, since each device may operate at different logic voltage levels:


Arduino = 5V

Raspberry/ESP = 3.3V

SOLUTION → Use a logic level translator (Level Shifter)

It may be **unidirectional** or **bidirectional**

 Example: BSS138 (bidirectional 3.3V <-> 5V)





Noise Margin

$$V_{NH} = V_{OH} - V_{iH}$$

$$V_{NL} = V_{iL} - V_{OL}$$

Example using two inverters:

  

Current Ratings


I_{iL} : Maximum LOW-level input current.

I_{iH} : Maximum HIGH-level input current.

I_{oL} : Maximum LOW-level output current.

I_{oH} : Maximum HIGH-level output current.

 
By convention, current flowing into the device is considered positive.



Parameter		Min	Nom	Max	Unit
I_{oH} : High Level Output current				-0.4	mA
I_{oL} : Low Level Output current				16	mA
	Test Conditions	Min	Typ	Max	
I_{iH}	$V_{CC} = \text{MAX } V_I = 2.4 \text{ V}$			40	μA
I_{iL}	$V_{CC} = \text{MAX } V_I = 0.4 \text{ V}$			-1.6	mA

Propagation Delay

$$t_{pd} = \frac{t_{PLH} + t_{PHL}}{2}$$

 

Parameter	From (Input)	To (Output)	Test Conditions	SN5404 SN7404			Unit
				Min	Typ	Max	
t_{PLH}	A	Y	$R_L = 400\Omega$ $C_L = 15pF$		12	22	ns
t_{PHL}					8	15	

Fan-out: Maximum number of equivalent logic inputs that can be driven by a single output.


Power Dissipation: Average power consumption under both HIGH and LOW logic states.

Speed–Power Product: The product of power dissipation (mW) and propagation delay (ns), expressed in picojoules (pJ). It is a useful figure of merit for applications requiring a balance between speed and power consumption..



Technologies (I)

Bipolar Logic Families

RTL
DTL
TTL
ECL

 



<http://youtu.be/Sxh4Vqe0sB4>

  

Technologies (II)


MOS Logic
Families

NMOS
PMOS
CMOS

  


TTL & CMOS

TTL NAND

 

CMOS NAND

 

<http://youtu.be/NHX-l-yHtDE>


<http://youtu.be/mnLFGk-tUtg>

BiCMOS

Combines:


- ❖ The high switching speed of bipolar output transistors.
- ❖ The low power dissipation of CMOS technology.

 The increased performance comes at the expense of greater circuit complexity.




<http://youtu.be/COTLXzm5ctg>


Evolution of Logic Families (I)

 


Texas Instruments Logic Guide 2014

 

Evolution of Logic Families (II)

 


Evolution of Logic Families (I)

 

Texas Instruments Little Logic Guide 2018

Output Stages (I)

Totem-Pole Output: Default output stage

 


<http://youtu.be/WqRMhfSYl1I>



Output Stages (II)

Open-Collector / Open-Drain Output

 


http://youtu.be/eIRzfj2IX_E

Requires an external pull-up resistor.
Supports wired-OR configurations.

Output Stages (III)

Three-State Output (Tri-State)

 

<http://youtu.be/iwjR9Kzt0cM>

Includes an enable input.

Allows the output to be disconnected by placing it in a high-impedance state.

References

- Texas Instruments Logic Guide: www.ti.com/logic